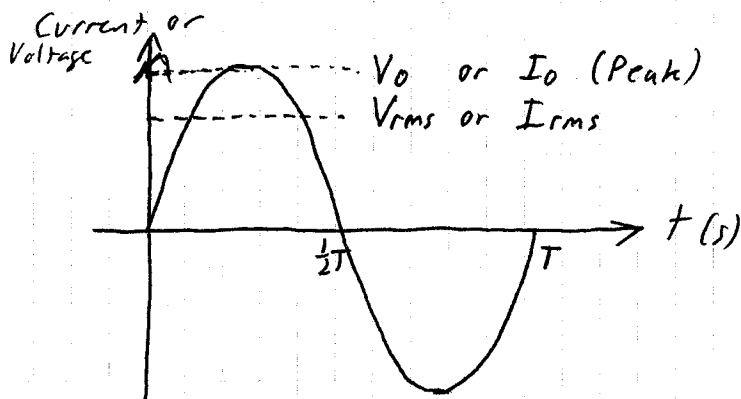


# Alternating Current (AC)

8-11-2005

AC 1



$$V = V_0 \sin(\omega t)$$

$$I = I_0 \sin(\omega t)$$

$$\omega = 2\pi f, \quad f = \frac{1}{T}$$

$V_0$ : Peak voltage  
 $I_0$ : Peak current

Time-average is defined as:  $\bar{y}(t) = \frac{1}{T} \int_0^T y(t) dt$ . (\*)

$$\bar{V} = 0 \text{ and } \bar{I} = 0 \text{ because } \frac{1}{T} \int_0^T \sin(\omega t) dt = 0.$$

It makes more sense then to define the rms-value (rms = "root-mean-square") or effective values:

$$\boxed{\begin{aligned} V_{rms} &= \sqrt{\overline{V^2}} = \frac{1}{\sqrt{2}} V_0 \\ I_{rms} &= \sqrt{\overline{I^2}} = \frac{1}{\sqrt{2}} I_0 \end{aligned}}$$

and because  $\frac{1}{T} \int_0^T \sin^2(\omega t) dt = \frac{1}{2}$ .

Power (for pure resistors +)

$$P = RI^2 = RI_0^2 \sin^2(\omega t). \quad \bar{P} = \frac{1}{2} RI_0^2 = R \cdot I_{rms}^2$$


$$P = \frac{V^2}{R} = \frac{1}{R} V_0^2 \sin^2(\omega t). \quad \bar{P} = \frac{1}{2} \frac{V_0^2}{R} = \frac{V_{rms}^2}{R}$$

$$P = V \cdot I = V_0 I_0 \sin^2(\omega t). \quad \bar{P} = \frac{1}{2} V_0 I_0 = V_{rms} I_{rms}$$

- that is, using rms-values (effective values) of  $V$  and  $I$  the formulas connecting  $\bar{P}$ ,  $V_{rms}$  and  $I_{rms}$  becomes identical with the DC-formulas.

+ [ $\bar{P}$ -formulas here only for resistors of the pure type - see Extra p.2]

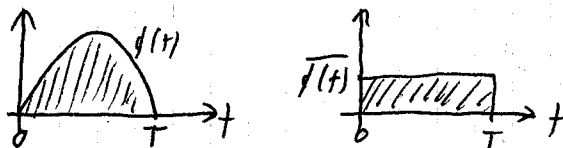(\*) As  $T \bar{y}(t) = \int_0^T y(t) dt$  the time-average can be illustrated by same areas:



Pure resistance, Ohm's law for AC-circuits


If the voltage and current of the component alternates in phase, that is:  $V = V_0 \sin(\omega t)$  and  $I = I_0 \sin(\omega t)$  then the component is a pure resistor with resistance  $R$ , and  $V = RI$  or  $V_0 = RI_0$  or  $V_{rms} = RI_{rms}$ .  
The power dissipated becomes:  $\bar{P} = V_{rms} I_{rms}$ .

Extra: Reactive components

For some components there will be a phase-shift between  $V$  and  $I$ :  $V = V_0 \sin(\omega t)$ ,  $I = I_0 \sin(\omega t - \varphi)$ .


Then it can be proved (using  $\sin(\omega t - \varphi) = \sin(\omega t)\cos(\varphi) - \cos(\omega t)\sin(\varphi)$ ) that  $\bar{P} = V_{rms} I_{rms} \cos \varphi$ .

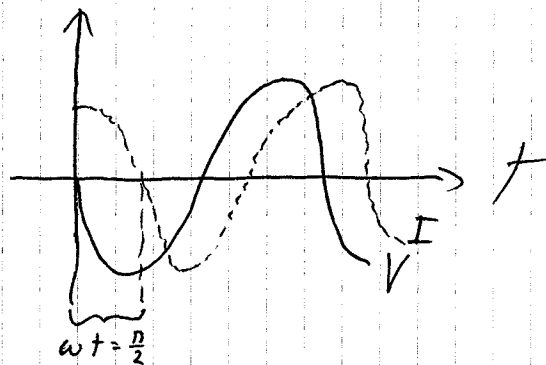For a coil of wire (an inductor)  $\varphi = \frac{\pi}{2}$  so that the current lags behind the voltage in time by a quarter of a cycle. The Power becomes:  $\bar{P} = 0$ , that is, no energy is dissipated in an ideal inductor.



When delivering AC-electricity, the power-plant must adjust its output so that the  $V_{rms} I_{rms}$  and the  $\varphi$  match the consumption-line.

## Transformation (Giancoli 21-7)

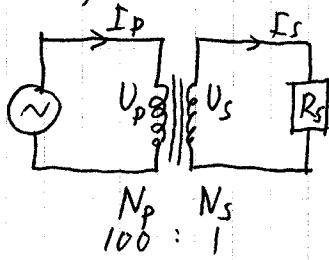

Faraday:

$$\left. \begin{aligned} \frac{V_s}{V_p} &= \frac{N_s}{N_p} \\ V_p I_p &= V_s I_s \end{aligned} \right\} \frac{I_s}{I_p} = \frac{N_p}{N_s}$$

No power-loss

From the primary side the resistance  $R_s$  creates the resistance:


$$R_p = \frac{V_p}{I_p} = V_p \times \frac{1}{I_p} = \frac{N_p}{N_s} V_s \times \frac{N_p}{N_s} \frac{1}{I_s} = \left(\frac{N_p}{N_s}\right)^2 \frac{V_s}{I_s}$$

that is:  $R_p = \left(\frac{N_p}{N_s}\right)^2 R_s$ .

Example:  $\frac{N_p}{N_s} = 100$ ,  $R_s = 0.1 \Omega$ . Then  $R_p = 1000 \Omega$

## Transmission of power by step-up and step-down Volt.

(Giancoli Ex. 21-10)

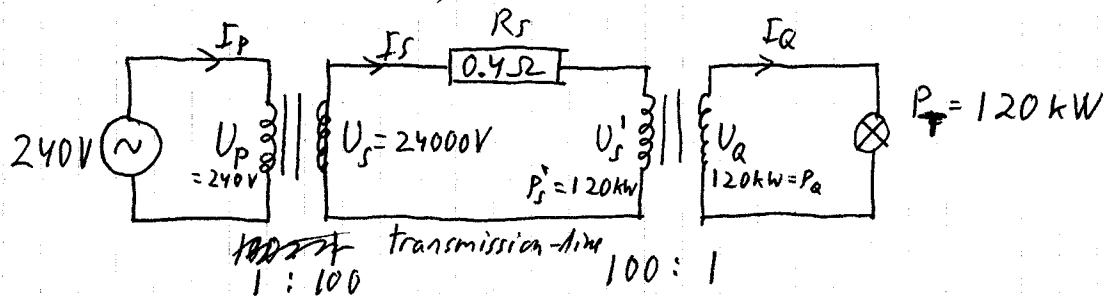

Power in transmission-line:

$$24000V \times I_s = 0.4 \Omega \cdot I_s^2 + 120 \text{ kW. Solve for } I_s.$$

Assuming  $0.4 \Omega \cdot I_s^2 \ll 120 \text{ kW}$ :  $I_s = \frac{24000V}{120 \text{ kW}} \frac{120 \text{ kW}}{24000V} = \underline{5A}$

Power-loss in transmission-line:  $0.4 \Omega \times I_s^2 = \underline{10W}$ .

(Usable solution of the quadratic equation:  $I_s = 5.00042A$ )

Power-loss without step-up, step-down:

$$I \approx \frac{120 \text{ kW}}{240V} = 500A. \quad 0.4 \Omega \times I^2 = \underline{100 \text{ kW}}$$